

# Course Code - CS223 Course Name - Digital Design

Section – 001

Lab Number – 04


Name Surname – Moin Khan

Student Id – 22101287


**Date** - 30/10/2023

#### 1. Resettable D Flip-Flop

```
1 timescale 1ps / 1ps
 5 module D_S_FF(input wire clk,
 6 | input wire reset,
 7 input wire d,
 8 output reg q);
10 \bigcirc always_ff @(posedge clk, posedge reset)
11 \ominus if (reset) q <= 1'b0;
12 else q <= d;
13 endmodule
`timescale 1ps / 1ps
module D_S_FF(input wire clk,
input wire reset,
input wire d,
output reg q);
always_ff @(posedge clk, posedge reset)
if (reset) q <= 1'b0;
else q \le d;
endmodule
```

 
 
#### 2. Circuit Schematic of Multi-Function Register



## 3. Structural System Verilog Module of Multi-Function Register

```
`timescale 1ps / 1ps

module MF_Register(input wire
d0,d1,d2,d3,s0,s1,shr_ln,shl_ln,reset,reg clk, output reg q0,q1,q2,q3);

reg w0,w1,w2,w3;

MUX_4To1 A(s1,s0,d0,shl_ln,q1,q0,w0);

MUX_4To1 B(s1,s0,d1,q0,q2,q1,w1);

MUX_4To1 C(s1,s0,d2,q1,q3,q2,w2);

MUX_4To1 D(s1,s0,d3,q2,shr_ln,q3,w3);

D_S_FF A1(clk,reset,w0,q0);

D_S_FF B1(clk,reset,w1,q1);

D_S_FF C1(clk,reset,w2,q2);

D S FF D1(clk,reset,w3,q3);
```

endmodule

### 4. Structural System Verilog Test-Bench for Multi-Function Register

```
`timescale 1ps / 1ps
module MF_Register_TB();
reg d0,d1,d2,d3,s0,s1,shr_ln,shl_ln,reset,clk;
wire q0,q1,q2,q3;
MF_Register test(d0,d1,d2,d3,s0,s1,shr_ln,shl_ln,reset,clk,q0,q1,q2,q3);
initial begin
    clk = 0;
    forever #10 clk = ~clk;
```

```
end
initial begin
assign d0 = 1'b1; assign d1 = 1'b1; assign d2 = 1'b1; assign d3 = 1'b1; assign shr_ln = 1'b1; assign shl_ln = 1'b0; #5;

assign reset =1'b0; assign s1 = 1'b1; assign s0 = 1'b1; #10; assign reset =1'b1; #5;
assign reset =1'b0; assign s1 = 1'b1; assign s0 = 1'b1; #10; assign reset =1'b0; assign s1 = 1'b0; assign s0 = 1'b0; #10; assign reset =1'b0; assign s1 = 1'b1; assign s0 = 1'b0; #10; assign reset =1'b0; assign s1 = 1'b1; assign s0 = 1'b1; #10;

$finish;
end
```

endmodule